


CS 223 Digital Design
Section:2
Laboratory Assignment 5

Alp Eren

Köken

22202876

1)

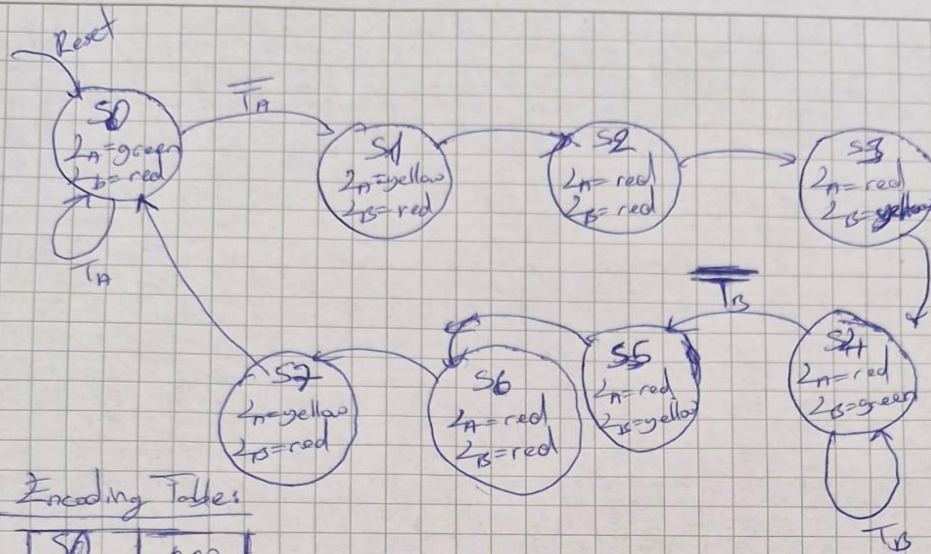

Encoding Tables:

S0	000
S1	001
S2	010
S3	011
S4	100
S5	101
S6	110
S7	111

State Table:

S2	S1	S0	Tn	Tb	S2'	S1'	S0'
0	0	0	0	X	0	0	1
0	0	1	1	X	0	0	0
0	1	0	X	X	0	1	0
0	1	1	X	X	0	1	1
1	0	0	X	0	1	0	1
1	0	1	X	1	1	0	0
1	1	0	X	X	1	1	0
1	1	1	X	X	0	0	0

$$S_2' = S_2 \bar{S}_1 + S_2 \bar{S}_0 + \bar{S}_2 S_1 S_0$$

Output Table:

S2	S1	S0	2A1	2A2	2B1	2B2
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	1
1	0	0	0	0	1	0
1	0	1	0	0	0	1
1	1	0	0	0	0	0
1	1	1	0	1	0	0

Output Encoding Table:

red	00
yellow	01
green	10

Equations:

$$S_2' = S_2 \bar{S}_1 + S_2 \bar{S}_0 + \bar{S}_2 S_1 S_0$$


$$S_1' = \bar{S}_1 S_0 + S_1 \bar{S}_0 = S_1 \oplus S_0$$

$$S_0' = S_1 \bar{S}_0 + \bar{S}_2 S_1 \bar{S}_0 T_n + S_2 \bar{S}_1 \bar{S}_0 T_b$$

$$2A1 = \bar{S}_2 \bar{S}_1 \bar{S}_0 \quad 2A2 = S_0 (S_2 \oplus S_1)$$

$$2B1 = S_2 \bar{S}_1 \bar{S}_0 \quad 2B2 = S_0 (S_1 \oplus S_1)$$

FSM:

 

2) Since we have 8 states, we can describe them with 3 flip-flops ($2^3=8$, S_2, S_1, S_0).

3) In Output Table for any S_2, S_1, S_0 condition, there is only one La_1, La_2, Lb_1, Lb_2 is 1 or none of them is one. So:

S_2	000	La_1
	001	La_2
	010	La_2
	011	La_2
S_1	100	Lb_1
	101	Lb_2
S_0	110	Lb_2
	111	Lb_2

4)

```
module trafficLights(input clk,reset,Ta, Tb,output La1, La2, Lb1, Lb2);
```

```
logic divided_clk;
```

```
wire S2,S1,S0,newS2,newS1,newS0;
```

```
clock_divider c(clk,divided_clk);
```

```
dFlipFlop d1(divided_clk,reset,newS2,S2);
```

```
dFlipFlop d2(divided_clk,reset,newS1,S1);
```

```

dFlipFlop d3(divided_clk,reset,newS0,S0);

assign newS2 = (S2&S1)|(S2&S0)|(S0&S1&S2);
assign newS1 = S1^S0;
assign newS0 = (S1&S0)|(Ta&S0&S1&S2)|(Tb&S0&~S1&S2);

assign La1 = (S0&S1&S2);
assign La2 = (S0&(S2^S1));
assign Lb1 = (S0&S1&S2);
assign Lb2 = (S0&(S1^S2));

endmodule

```

```

module clock_divider(
    input logic clk,
    output logic newClk
);

    logic [26:0] count;

    always_ff @(posedge clk)begin
        if (count<100000000 - 1)
            count <= count + 1;
        else begin
            newClk <= ~ newClk;
            count <= 0;
        end
    end

endmodule

```

```
module dFlipFlop(  
    input logic clk,  
    input logic reset,  
    input logic D,  
    output logic Q  
);  
  
always_ff @(posedge clk)  
if(reset) Q <= 0;  
else Q <= D;  
  
endmodule
```

Testbench:

```
module trafficLights_tb;  
  
    reg clk,reset,Ta,Tb;  
    wire La1, La2, Lb1, Lb2;  
  
    trafficLights dut(clk,reset,Ta,Tb,La1,La2,Lb1,Lb2);  
  
    initial clk = 0;  
    always #5 clk = ~clk;  
  
    initial begin  
        reset = 1;  
        Ta = 0;  
        Tb = 0;  
        #20 reset = 0;  
        #50 Ta = 1;
```



```

#50 Ta = 0;
#50 Tb = 1;
#50 Tb = 0;
#200;

end
endmodule

```

5)

In terms of recursion, we are gonna use n-1 bit gray code to generate n bit gray code. If we shift n-1 bit gray codes 1 bit to right and add appropriate bit to missing MSB, we will be done. Normally, we put 0 to MSB and get first half of the n bit gray codes. Then, we put 1 to MSB, but this time we must use (n-1)-bit gray codes in the reverse order.

To make these process shorter we can XOR the binary code value with its 1 bit right-shifted version. This converts the binary counter value into an equivalent Gray Code.

6)

```

module grayCode4(input clk, reset, en, load, input logic [3:0] pLoad, output logic [3:0] result);
    logic [3:0] code;
    always_ff @(posedge clk or posedge reset) begin
        if (reset)
            code<=4'b0000;
        else if (load && en)
            code<=pLoad;
        else if (en)
            code<=code+1;
    end
    assign result = code^(code >> 1);

endmodule

```

Testbench:

```

module grayCode4_tb;

```

```
reg clk,reset,en,load;  
logic [3:0] pLoad;  
logic [3:0] result;  
grayCode4 dut (clk,reset,en,load,pLoad,result);
```

```
initial clk = 0;  
always #5 clk = ~clk;
```

```
initial begin
```

```
    reset = 1;  
    en = 0;  
    load = 0;  
    pLoad = 4'b0000;
```

```
    #10 reset = 0;
```

```
    #10 load = 1; pLoad = 4'b1010;  
    #10 load = 0;
```

```
    #10 en = 1;  
    #40 en = 0;
```

```
    #10 load = 1; pLoad = 4'b1100;  
    #10 load = 0;
```

```
    #10 en = 1;  
    #40 en = 0;
```

```
    #10 reset = 1;  
    #10 reset = 0;
```

```

        #20;

    end

endmodule

7)

module grayCode8(input clk, reset, en, load,input logic [7:0] pLoad,output logic [7:0] result);

    logic [7:0] code;

    always_ff @(posedge clk or posedge reset) begin
        if (reset)
            code<=8'b00000000;
        else if (load && en)
            code<=pLoad;
        else if (en)
            code<=code+1;
    End

    assign result = code^(code >> 1);

endmodule

```

TestBench:

```

module grayCode8_tb;

    reg clk, reset, en, load;

    logic [7:0] pLoad;
    logic [7:0] result;

    grayCode8 dut (clk, reset, en, load, pLoad, result);

```



```
initial clk = 0;
```

```
always #5 clk = ~clk;
```

```
initial begin
```

```
    reset = 1;
```

```
    en = 0;
```

```
    load = 0;
```

```
    pLoad = 8'b00000000;
```

```
    #10 reset = 0;
```

```
    #10 load = 1; pLoad = 8'b10101010;
```

```
    #10 load = 0;
```

```
    #10 en = 1;
```

```
    #80 en = 0;
```

```
    #10 load = 1; pLoad = 8'b11001100;
```

```
    #10 load = 0;
```

```
    #10 en = 1;
```

```
    #80 en = 0;
```

```
    #10 reset = 1;
```

```
    #10 reset = 0;
```

```
    #20;
```

```
end
```

endmodule